
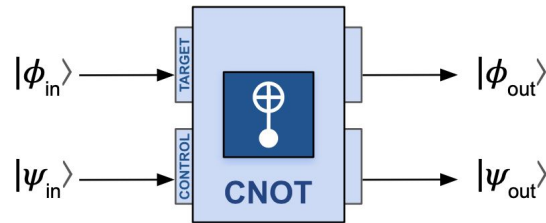


# Practice Questions: Inverting gates

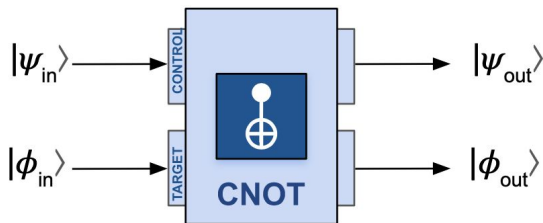1) True or False: These two circuits have the same matrix.



2) True or False: These two circuits have the same matrix.

