

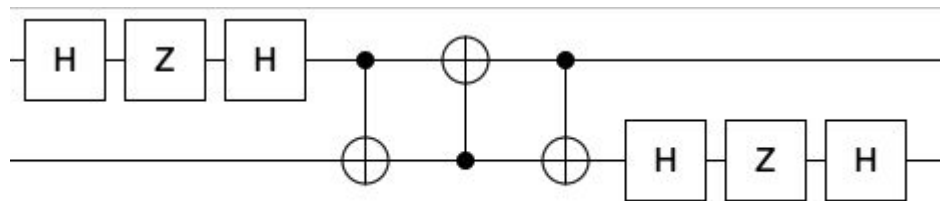


# Practice Questions: Identities/Commutative Rules

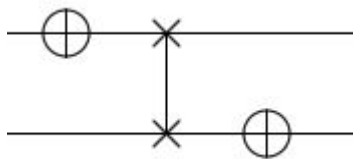1) True or False: These circuits are equivalent.



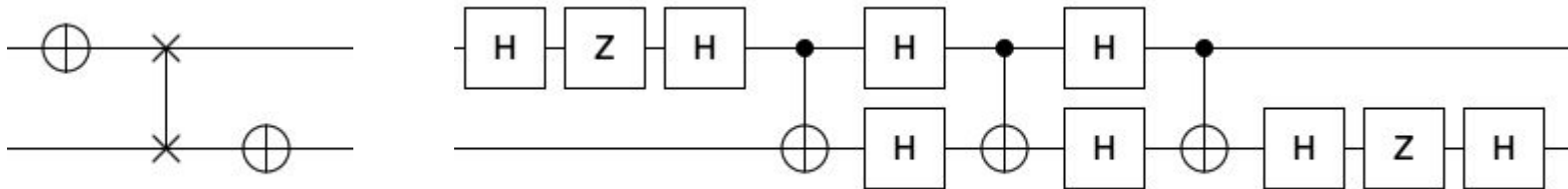2) True or False: These circuits are equivalent



3) True or False: These two circuits are equivalent.

