

Advanced Operations

homework

True/False

This state evolution table represents an inverted CNOT gate.

State Evolution:

$$|\text{target}\rangle \otimes |\text{control}\rangle \mapsto |\text{target}\rangle \otimes |\text{control}\rangle$$

$$|\phi_{\text{in}}\rangle \otimes |\psi_{\text{in}}\rangle \mapsto |\phi_{\text{out}}\rangle \otimes |\psi_{\text{out}}\rangle$$

$$|0\rangle \otimes |0\rangle = |00\rangle \mapsto |0\rangle \otimes |0\rangle = |00\rangle$$

$$|0\rangle \otimes |1\rangle = |01\rangle \mapsto |1\rangle \otimes |1\rangle = |11\rangle$$

$$|1\rangle \otimes |0\rangle = |10\rangle \mapsto |1\rangle \otimes |0\rangle = |10\rangle$$

$$|1\rangle \otimes |1\rangle = |11\rangle \mapsto |0\rangle \otimes |1\rangle = |01\rangle$$

True/False:


Two-qubit gates can be placed on quantum circuits in any order. FALSE

No matter how you place a gate on a multi-qubit quantum circuit, you will get the same result. FALSE

Any quantum gate can be made into the target part of a larger controlled gate. TRUE

Circuit Transformation HOMEWORK

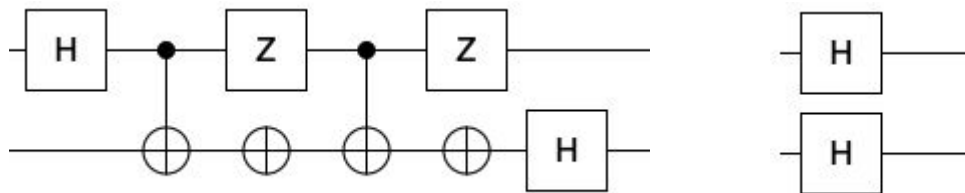(True / False) These circuits are equivalent.



Which circuit is not equivalent to the rest?

